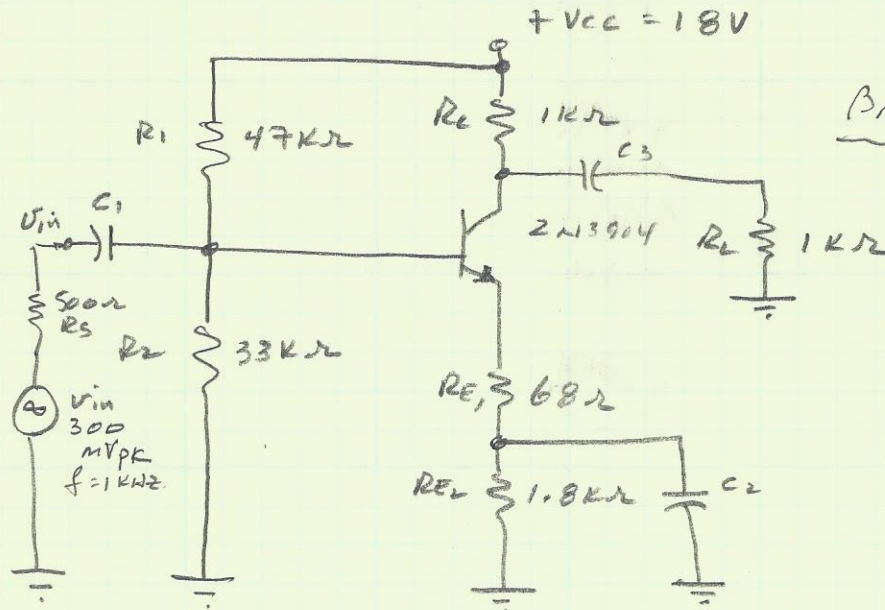


BJT CE AMPLIFIER ANALYSIS EXAMPLE - DC + AC (w/ SWAPPING)



$$\beta_{AC} = \beta_{DC} = 150$$

$$C_1 = C_3 = 100\mu F$$

$$C_2 = 47\mu F$$

DC (BIAS + Q-POINT) ANALYSIS FIRST: [V-DIVIDER BIAS]

$$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$V_B = \left(\frac{33k\Omega}{80k\Omega} \right) 18V$$

$$V_B = 7.425V$$

$$V_E = V_B - V_{BE} \quad \rightarrow 0.7V$$

$$V_E = 6.725V$$

$$I_E = \frac{V_E}{R_E + R_{EE}}$$

$$\frac{6.725V}{68\Omega + 1.8k\Omega}$$

$$I_E = 3.6mA$$

$$I_E \approx I_C = 3.6mA$$

$$\uparrow$$

$$I_{CQ}$$

$$r'_e = \frac{25mV}{I_E}$$

$$= \frac{25mV}{3.6mA}$$

$$r'_e = 6.944\Omega$$

$$V_{RC} = I_C \cdot R_C$$

$$= (3.6mA) 1k\Omega$$

$$V_{RC} = 3.6V$$

$$V_C = V_{CC} - V_{RC} \quad \rightarrow (I_C \cdot R_C)$$

$$= 18 - 3.6V$$

$$V_C = 14.4V$$

$$V_{CE} = V_C - V_E$$

$$= 14.4 - 6.725V$$

$$V_{CE} = 7.675V_{DC}$$


$$\leftarrow V_{CEQ}$$

$$I_{C(SAT)} = \frac{V_{CC} - 0.7}{R_C + R_E + R_{EE}} = \frac{17.3V}{2.868k\Omega}$$

$$I_{C(SAT)} = 6.032mA$$

AC ANALYSISAC EQUIVALENT CIRCUIT :

(WITH INPUT SOURCE):

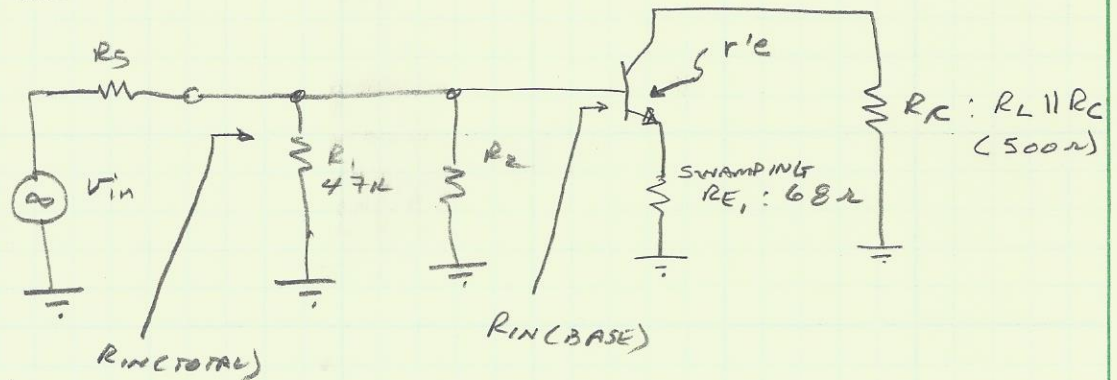

$$R_{IN(BASE)} = \beta_{AC} (r'_e + R_{E1})$$

(w/o SWAMPING, i.e. RE COMPLETELYBYPASSED): $R_{IN(BASE)} = \beta_{AC} \cdot r'_e$

$$R_{IN(BASE)} = 150 (6.944 + 68\Omega)$$

$$R_{IN(BASE)} = 11.242 \text{ k}\Omega$$

$$R_{IN(TOTAL)} = R_1 \parallel R_2 \parallel R_{IN(BASE)}$$

$$= 47\text{k}\Omega \parallel 33\text{k}\Omega \parallel 11.242 \text{ k}\Omega$$

$$R_{IN(TOTAL)} = 7.116 \text{ k}\Omega$$

$$R_{OUT} = R_{LOAD(AC)} = R_C = R_L \parallel R_C$$

$$R_C = 1\text{k}\Omega \parallel 1\text{k}\Omega ; \quad R_C = 500\Omega$$

AC ANALYSIS (CONTINUED):VOLTAGE GAIN: A_V (RAW; W/O ATTENUATION)

$$A_V = \frac{R_C}{r_E + R_{E1}}$$

$$= \frac{500\Omega}{6.9 + 68}$$

$$A_V = 6.68$$

note: SCALAR QTY
NO DIMENSIONSATTENUATION:

$$\text{ATTENUATION} = \frac{V_A}{V_B} = \frac{R_A + R_{in}(\text{TOTAL})}{R_{in}(\text{TOTAL})}$$

$$= \frac{500\Omega + 7.116\text{k}\Omega}{7.116\text{k}\Omega}; \quad \text{ATTN} = 1.07$$

REAL VOLTAGE GAIN (ACTUAL CONSIDERING ATTENUATION)ATTN IS 1.07. REAL GAIN IS RAW GAIN
TIMES THE RECIPROCAL OF THE ATTENUATION.

$$\therefore A'_V = A_V \cdot \frac{1}{\text{ATTN}}$$

$$A'_V = (6.68)0.934$$

$$A'_V = 6.235$$

$$\text{SO: } V_{out} = A'_V \cdot V_{in} \\ = 6.235 \cdot 300\text{mV}_{pk}$$

$$V_{out_{pk}} = 1.875\text{V}_{pk}$$

OR: in rms values

$$V_{out_{rms}} = 1.322\text{V}_{rms}$$

AC ANALYSIS (CONTINUED):

$$I_A = \frac{V_s}{R_s + R_{in(TOTAL)}} = \frac{1.322 \text{ V}_{rms}}{500\Omega + 7.116\text{k}\Omega}$$

$$I_b = 174\mu\text{A}$$

CURRENT GAIN:

$$A_i = \frac{I_C}{I_A} = \frac{(1.322 \text{ V}_{rms} / 500\Omega)}{174\mu\text{A}}$$
$$= \frac{2.644\text{mA}}{0.174\text{mA}}$$

$$A_i \approx 15.2$$

POWER GAIN

$$A_P = A_v' A_i$$
$$= (6.235)(15.2)$$

$$A_P = 94.74$$