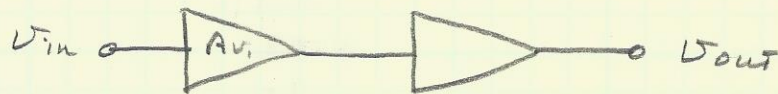


6-6 MULTISTAGE AMPLIFIERS

(P. 301)

- "CASCADED AMPLIFIERS"
- GAIN IS PRODUCT OF INDIVIDUAL STAGES
- SYMBOLOLOGY OF AN AMP STAGE IS A "TRIANGLE,"



$$A_{V(TOTAL)} = A_{V1} \cdot A_{V2}$$

$$V_{out} = A_{V(TOTAL)} \cdot V_{in}$$

- DECIBELS

$$A_V(dB) = 20 \log_{10} A_V$$


CAPACITIVELY COUPLED MULTI-STAGE AMP

(P. 302)

-(SEE FIG. 6-34 P. 302)

TO GET VOLTAGE GAIN OF STAGE #1: CONSIDER
LOADING EFFECT ON STAGE #1 OF STAGE 2.

AC EQUIVALENT OF FIRST STAGE:

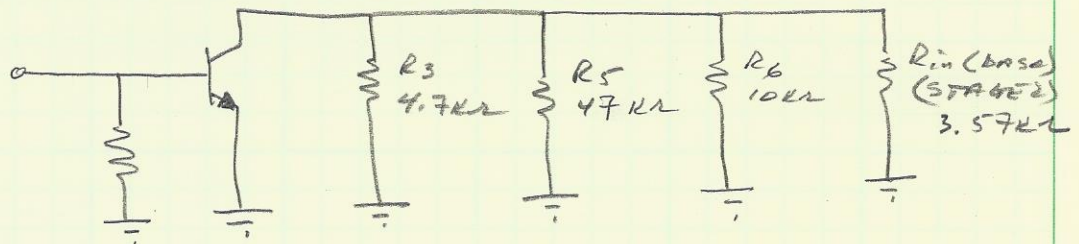

SO, EFFECTIVE COLLECTOR RESISTANCE (AC-WISE)
OF Q1 IS:

$$R_{C1} = R_3 \parallel R_5 \parallel R_6 \parallel R_{in(BASE2)}$$

ALL IN PARALLEL TO AC GROUND.

BY ANALYSIS, LOOKING AT STAGE 2 TO
FIND $R_{in}(BASE2)$:

STAGES
ARE IDENTICAL

$$V_B = \left(\frac{10}{57}\right) 10V; V_B = 1.75V$$

$$V_E = 1.75 - 0.7; V_E = 1.05V$$

SO DC
VALUES
ARE SAME

$$\text{THEN: } I_{E2} = 1.05V / 1k; \boxed{I_{E2} = 1.05mA}$$

$$r'_e = \frac{25mV}{I_E}; \therefore \boxed{r'_e = 23.81\Omega}$$

NOW, $R_{in}(BASE2)$:

$$R_{in}(BASE2) = \beta_{AC} r'_e \quad (R_E \text{ IS BYPASS; NO SWAMPING } R_E)$$

$$R_{in}(BASE2) = 150(23.81\Omega)$$

$$\boxed{R_{in}(BASE2) = 3.571k\Omega}$$

$$\text{THEREFORE, } R_{C1} = R_3 \parallel R_5 \parallel R_6 \parallel R_{in}(BASE2)$$

$$= 4.7k\Omega \parallel 47k\Omega \parallel 10k\Omega \parallel 3.571k\Omega$$

$$\boxed{R_{C1} \approx 1.63k\Omega} \quad (1.6285k\Omega)$$

GAINS:

$$\text{STAGE \#1: } A_{V1} = \frac{R_{C1}}{r'_e} = \frac{1.63k\Omega}{23.8\Omega}$$

$$\boxed{A_{V1} = 68.5}$$

STAGE \#2:

$$A_{V2} = \frac{R_7}{r'_e} \quad \text{"} R_{C2} \text{"}$$

$$= \frac{4.7k\Omega}{23.8\Omega}$$

$$\boxed{A_{V2} = 197}$$

OVERALL VOLTAGE GAIN

$$A_{V(TOTAL)} = A_{V1} \cdot A_{V2}$$

$$= (68.5)(197)$$

$$A_{V(TOTAL)} = 13,521$$

$$dB = 20 \log_{10} A_{V(TOTAL)}$$

$$= 20 \log_{10} (13521)$$

$$= 20(4.131)$$

$$A_{V(TOTAL)} dB = 82.62 dB$$

TYPICAL PROCESS:

- DETERMINE "TYPE" OF AMPLIFIER IN EACH STAGE:
 - CE: WILL HAVE A GAIN
 - COMMON COLLECTOR (EMITTER FOLLOWER) AND COMMON BASE TOPOLOGIES WILL HAVE UNITY GAIN (i.e., $A_V = 1$)
- DC ANALYSIS OF EACH STAGE
- AC ANALYSIS: GET GAINS
- TOTAL GAIN IS PRODUCT OF STAGE GAINS.