

6-4 COMMON-COLLECTOR AMPLIFIER - Emitter, Input

P. 291


- O/P IN  $\phi$  W/ INPUT!
- TAKEN FROM EMITTER.

Followed

## DC ANALYSIS - NOTE:

NO  $R_c$ : OTHERWISE  
SAME AS C-F  
AMP.

W/V-DIVIDE  
BIAS.

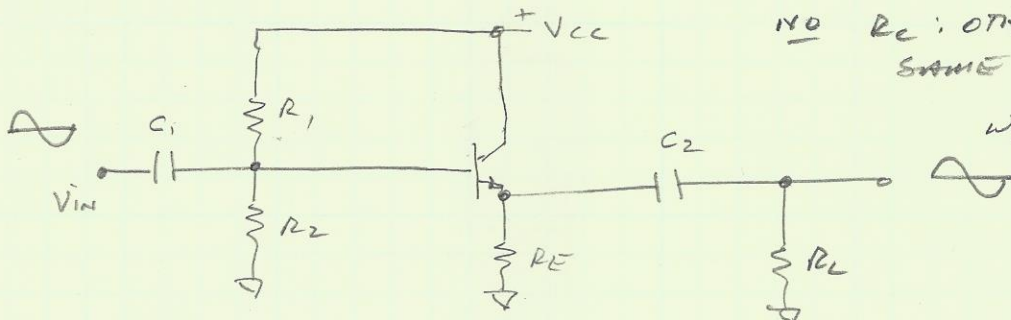

# AC ANALYSIS

VOLTAGE GAIN

p. 292

$$Av \approx 1$$

$$R_E \parallel R_L$$

### INPUT RESISTANCE

$$R_{in}(base) \approx \beta_{ac} R_e$$

$$R_{in}(tot) = R_1 \parallel R_2 \parallel R_{in}(base)$$

OUTPUT      RESISTANCE

$$R_{out} \approx \left( \frac{R_s}{\beta_{ac}} \right) \parallel R_E$$

CURRENT GAIN

$$A_i = \frac{I_e}{I_{in}}$$

POWER GAIN

$$A_p \approx A_i \quad (\text{since } A_v \approx 1)$$

- see ex 6-9 p. 294.


DARLINGTON PAIR p. 295

$-\beta_{ac}$ : MAJOR FACTOR IN DETERMINING  
INPUT RESISTANCE OF AN AMPLIFIER


INPUT RESISTANCE CAN BE INCREASED  
VIA A "DARLINGTON" PAIR

$$R_{in} = \beta_{ac1} \beta_{ac2} R_E$$

"SQUARE OF THE  
GAINS!"

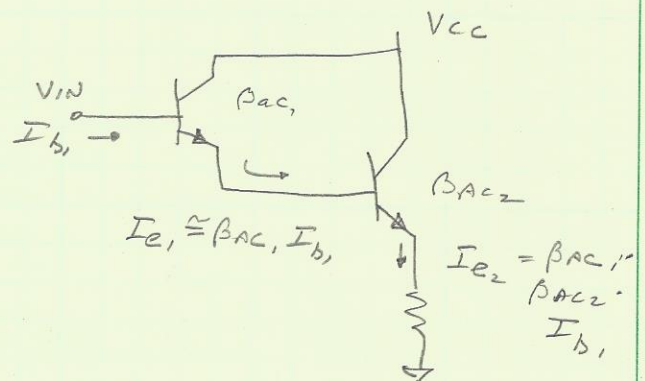6-5 COMMON BASE AMPLIFIER

(BASE IS @ COMMON OR AC GROUND)

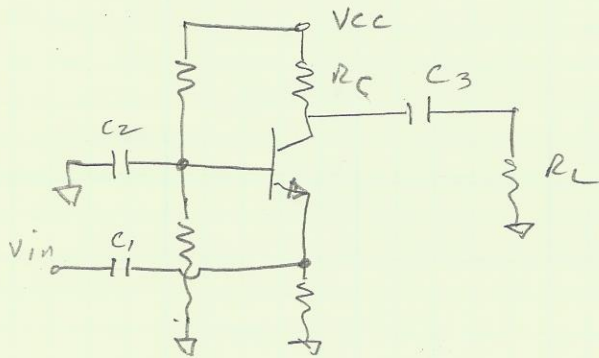

O/P IN  $\phi$  w/ input

INPUT RESISTANCE

$$R_{in(emitter)} \approx r'_e$$

O/P RESISTANCE

$$R_{out} \approx R_C$$

CURRENT GAIN


$$A_i \approx 1$$

POWER GAIN

$$A_p = A_v$$



## COMMON EMITTER EXAMPLE

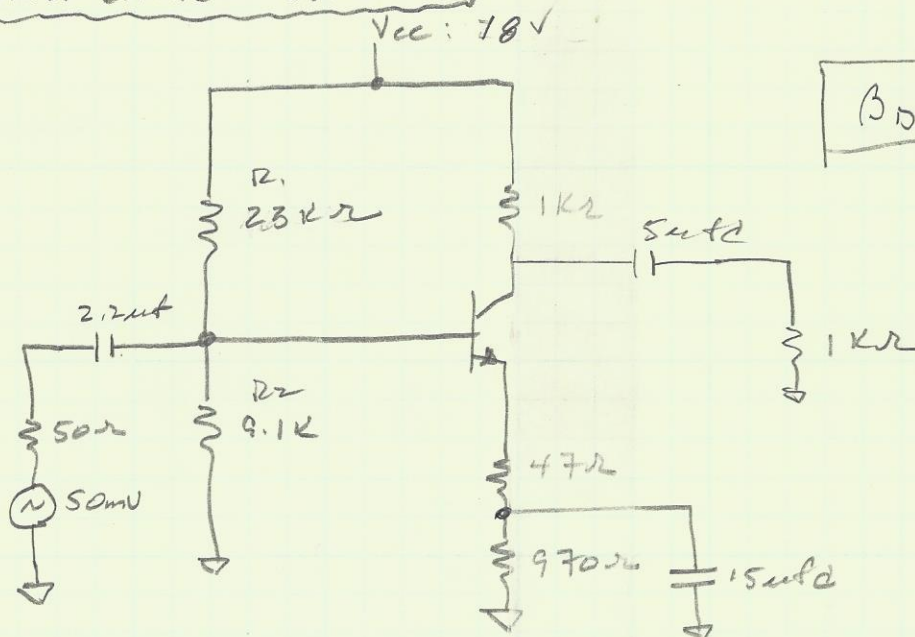

$$\beta_{DC} = \beta_{AC} = 185$$

DC ANALYSIS

$$① V_B = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{9.1\text{ k}\Omega}{(23 + 9.1)\text{ k}\Omega} \right) 18\text{ V} = 0.28(18)$$

$$V_B = 5.1\text{ V}$$

$$② V_E = V_B - V_{BE} = 5.1 - 0.7$$

$$V_E = 4.4\text{ V}$$

$$③ I_E = \frac{V_E}{R_E + R_{E2}} = \frac{4.4\text{ V}}{47\text{ }\Omega + 970\text{ }\Omega}$$

$$I_E = 4.3\text{ mA}$$

$$④ I_E \approx I_C \approx 4.3\text{ mA}$$

$$\begin{aligned} ⑤ V_C &= V_{CC} - I_C R_C \\ &= 18\text{ V} - (4.3\text{ mA})(1\text{ k}\Omega) \\ &= 18\text{ V} - 4.3\text{ V} \end{aligned}$$

$$V_C = 13.7\text{ V}$$

$$\begin{aligned} ⑦ I_{C(sat)} &= \frac{V_{CC} - V_{BE}}{R_C + R_E + R_{E2}} \\ &= \frac{18\text{ V} - 0.7\text{ V}}{1\text{ k}\Omega + 47\text{ }\Omega + 970\text{ }\Omega} \end{aligned}$$

$$I_{C(sat)} = \frac{17.3\text{ V}}{2.017\text{ k}\Omega}$$

$$I_{C(sat)} = 8.6\text{ mA}$$

$$⑧ V_{CEQ} = 18\text{ V}$$

$$\begin{aligned} ⑥ V_{CE} &= V_C - V_E \\ &= 13.7\text{ V} - 4.4\text{ V} \end{aligned}$$

$$V_{CE} = 9.3\text{ V}$$



COMMON EMITTER EXAMPLEAC ANALYSIS

$$① \quad r'_e = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{4.3 \text{ mA}}$$

$$\boxed{r'_e = 5.81 \Omega}$$

$$② \quad R_{in}(\text{base}) = \beta_{ac}(r'_e + R_{E1})$$

$$= 185(5.81 \Omega + 47 \Omega)$$

$$\boxed{R_{in}(\text{base}) = 9.77 \text{ k}\Omega}$$

$$③ \quad R_{in}(\text{total}) = R_1 \parallel R_2 \parallel R_{in}(\text{base})$$

$$= 23 \text{ k}\Omega \parallel 9.1 \text{ k}\Omega \parallel 9.77 \text{ k}\Omega$$

$$\boxed{R_{in}(\text{total}) = 3.91 \text{ k}\Omega}$$

$$④ \quad A_v = \frac{R_C \parallel R_L}{R_{E1}} = \frac{1 \text{ k}\Omega \parallel 1 \text{ k}\Omega}{47 \Omega} = \frac{500 \Omega}{47 \Omega}$$


$$\boxed{A_v \approx 10.62}$$

$$⑤ \quad V_{out} = A_v \cdot V_{in}$$

$$= 10.62 \cdot 50 \text{ mV}$$

$$\boxed{V_{out} = 0.532 \text{ V}}$$

## EMITTER FOLLOWER EXAMPLE

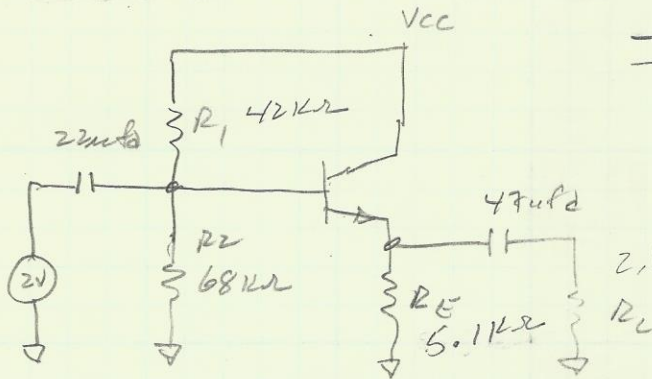

$$\beta_{dc} = \beta_{ac} = 190$$

## - DC ANALYSIS

$$\textcircled{1} V_B = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{68k\Omega}{42k\Omega + 68k\Omega} \right) 18V$$

$$V_B = 11.13V_{DC}$$

$$\textcircled{2} V_E = V_B - V_{BE} = 11.13V_{DC} - 0.7V$$

$$V_E = 10.43V_{DC}$$

$$\textcircled{3} I_E = I_C = \frac{V_E}{R_E} = \frac{10.43V}{5.1k\Omega}$$

$$I_E = 2.05mA$$

$$\textcircled{4} V_{CE} = V_{CC} - V_E = 18V - 10.43V_{DC}$$

$$V_{CE} = 7.57V_{DC}$$


$$\textcircled{5} I_{C(SAT)} = \frac{V_{CC} - V_{BE}}{R_E} = \frac{18V - 0.7V}{5.1k\Omega}$$

$$I_{C|SAT} = 3.39mA$$

$$V_{CEC-0} = 18V$$

# EMITTER FOLLOWER EXAMPLE (CONTINUED)

## AC ANALYSIS

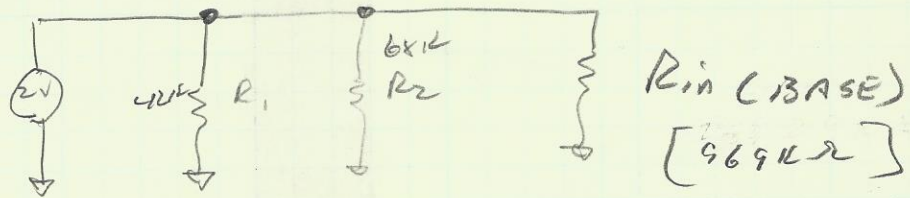

$$\begin{aligned}
 R_{in}(base) &= \beta_{ac} R_E \\
 &= 190 \cdot 5.1k\Omega \\
 &= 969k\Omega
 \end{aligned}$$

$$\begin{aligned}
 R_{in}(tot) &= R_1 \parallel R_2 \parallel R_{in}(base) \\
 &= (42k\Omega^{-1} + 68k\Omega^{-1} + 969k\Omega^{-1})^{-1} \\
 &= 25.29k\Omega
 \end{aligned}$$

$$A_v = 1$$

$$V_{out} \approx 2V$$