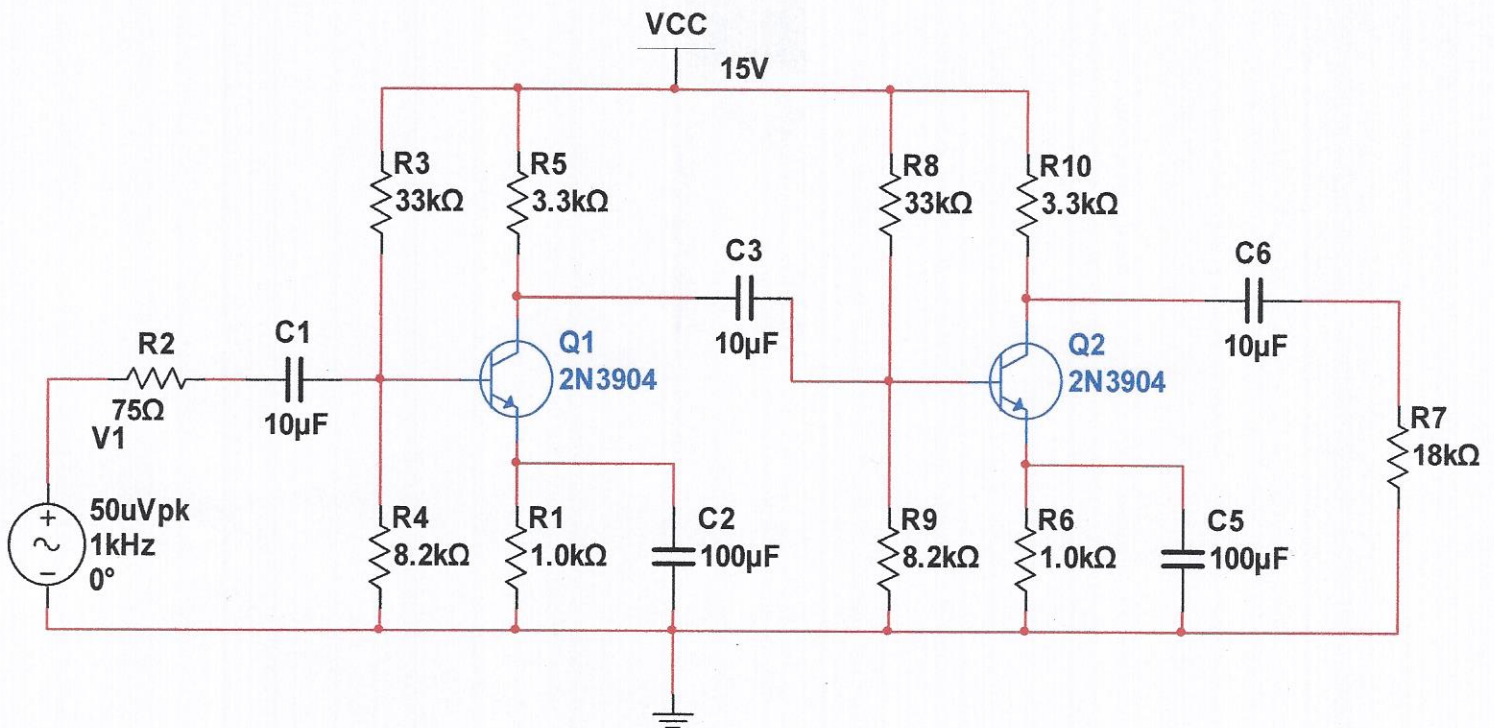


Mutli-stage (two-stage Cascaded Common-Emitter) Amplifier - EXAMPLE

$V_{in} = 50 \mu V$ pk; $\beta_{dc} = \beta_{AC} = 175$.



ANALYSIS PROCESS

- NEED TO KNOW "LOAD" ON STAGE 1 (LEFTMOST STAGE). LOAD ON STAGE 1 IS $R_{in(TOTAL)2}$; $R_{in(TOTAL)}$ FOR SECOND STAGE.

- SO FOR STAGE 2: (DC ANALYSIS):

$$V_{B2} = \left(\frac{R_9}{R_8 + R_9} \right) V_{CC}; \boxed{V_{B2} = 2.98V_{DC}}; V_{E2} = 2.98V_{DC} - 0.7; \boxed{V_{E2} = 2.285V_{DC}}$$

$$I_{E2} \approx I_{C2} = V_{E2}/R_6; \boxed{I_{E2} \approx I_{C2} = 2.285mA}; r'_{e2} = \frac{25mV}{I_{E2}}; \boxed{r'_{e2} = 10.94\Omega}$$

- FINALLY, FOR STAGE 2: "AC ANALYSIS - START"

$$R_{in(BASE)2} = \beta_{AC2} \cdot r'_{e2}; R_{in(BASE)2} = (175)(10.94\Omega)$$

$$\boxed{R_{in(BASE)2} = 1.915K\Omega}$$

$$R_{in(TOTAL)2} = R_8 \parallel R_9 \parallel R_{in(BASE)2};$$

$$\boxed{R_{in(TOTAL)2} = 1.483K\Omega}$$

$$R_{C2} = R_{10} \parallel R_7; \boxed{R_{C2} = 2.789K\Omega}$$

$$\boxed{R_{C2} = 2.789K\Omega}$$

- NOW, STAGE 1:

- DC ANALYSIS (STAGES ARE IDENTICAL, SEE STAGE 2 CALCULATIONS).

- $R_{C1} = R_5 \parallel R_L$ $\leftarrow R_L \text{ IS } R_{IN(TOTAL)2}!$

$$= 3.3\text{k}\Omega \parallel 1.483\text{k}\Omega ;$$

$$R_{C1} = 1.023\text{k}\Omega$$

- $R_{IN(BASE)1} = 1.915\text{k}\Omega$ (SAME AS STAGE 2)

- $R_{IN(TOTAL)1} = 1.483\text{k}\Omega$ (SAME AS STAGE 2)

- GAINS

$$A_{V1} = \frac{R_{C1}}{r_{e1}} = \frac{1.023\text{k}\Omega}{10.94\Omega} ; \quad A_{V1} = 93.5$$

$$A_{V2} = \frac{R_{C2}}{r_{e2}} = \frac{2.789\text{k}\Omega}{10.94\Omega} ; \quad A_{V2} = 255$$

$$A'_{V(TOTAL)} = A_{V1} \cdot A_{V2} \cdot \text{ATTN}^{-1}$$

$$\text{ATTN} = \frac{R_A + R_{IN(TOTAL)1}}{R_{IN(TOTAL)1}} = \frac{75\Omega + 1.483\text{k}\Omega}{1.483\text{k}\Omega}$$

$$\text{ATTN} = 1.056 ; \quad (\text{ATTN}^{-1}) = 0.9519$$

$$\therefore A'_{V(TOTAL)} = A_{V1} \cdot A_{V2} \cdot \text{ATTN}^{-1}$$

$$= (93.5)(255)(0.9519) ; \quad A'_{V(TOTAL)} = 22694$$

$$V_{OUT} = V_{IN} \cdot A'_{V(TOTAL)}$$

$$= 50\text{mV} \cdot 22694 ;$$

$$V_{OUT} = 1.135\text{V}_{PK}$$

$$\text{GAIN(dB)} = 20 \log_{10} A'_{V(TOTAL)}$$

$$A'_{V(TOTAL)|dB} = 20 \log_{10}(22694) ;$$

$$A'_{V(TOTAL)|dB} = 87.1\text{dB}$$